

TOWARDS MASTERING DC & AC circuits


- ① Explore common circuit elements in a DC setting (resistor, capacitor, inductor)
- ② Gain insight into circuit element behavior in AC setting (phasor language, impedance)

DC circuits: circuits in which DIRECTION of current unchanged

source of current: battery providing a voltage/potential difference/electromotive force \mathcal{E} . "pumps charges against existing potential differences".

RESISTORS: Element made of a material for which "Ohm's law" holds. When potential difference is applied a constant current ensues $I = \Delta V \cdot 1/R$ (R resistance [R]= Ω)

Microscopic picture: Current density $\vec{J} = nq\vec{v}$ $|\vec{J}| = \frac{I}{A}$
induced by presence of an electric field $|\vec{J}| = \sigma |\vec{E}|$
(σ conductivity, property of material) general Ohm's law

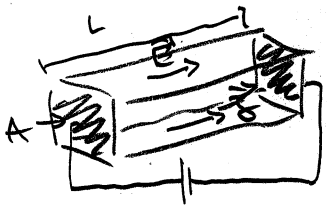

if we assume constant \vec{E} inside material
 $\Delta V = \vec{E} \cdot L$ $|\vec{J}| = \frac{I}{A} = \sigma \frac{\Delta V}{L} \Rightarrow I = \frac{\Delta V}{\frac{L}{\sigma A}} = \frac{\Delta V}{R}$


Think about: $\vec{F}_e = q\vec{E}$ if \vec{E} constant \Rightarrow Newton's 2nd law
 $\Rightarrow \vec{a} = \text{const.} \Rightarrow \vec{v}(t) = \vec{v}_0 + \vec{a}t$ increases, so why $\vec{J} \times \vec{v} = \text{const.}$?

Reason: electrons in the material bump into each other and the crystal grid \rightarrow motion becomes randomized. Work done by \vec{E} on charges \rightarrow converted to heat.



"Resistors dissipate power as heat", "Charges moving through resistor lose some electric potential energy"

How much power? $E_{el} = Q \cdot V$
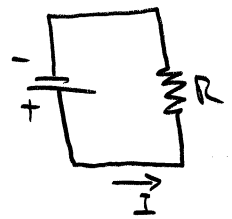
$$\frac{d}{dt} E_{el} = P_{el} = \frac{dQ}{dt} \cdot V = I \cdot V = I^2 R = V^2 / R$$




You are familiar with:

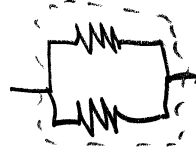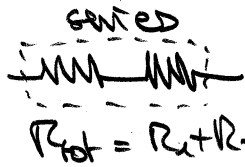


$$1/R_{tot} = 1/R_1 + 1/R_2$$

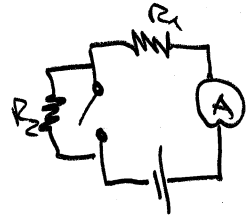Quick refresher: what happens to \textcircled{A} if switch is open? $I = \Delta V / R_1 + R_2$ if closed $I = \Delta V / R_1$



Reducing circuits with symmetry:

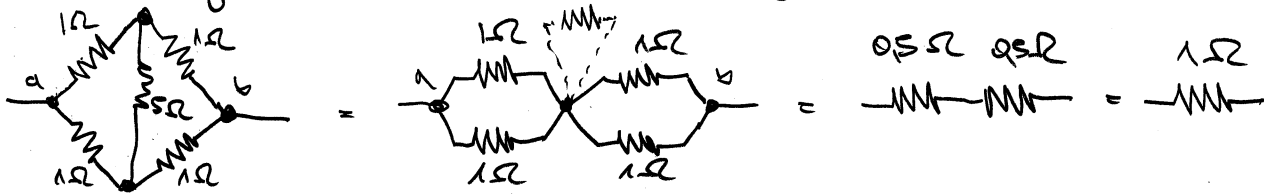

Since all resistors 1Ω on outside $I_{ac} = I_{ad} \Rightarrow \Delta V_{ac} = \Delta V_{ad}$
 $\Rightarrow \Delta V_{cd} = 0 \Rightarrow I_{cd} = 0$

further study: Thevenin's theorem - Any circuit made solely of resistors and batteries is EQUIVALENT to a single voltage source and a single resistor.

KIRCHHOFF'S RULES: (I) JUNCTION RULE: zero NET current flow into any node $\sum I_{in} = \sum I_{out}$
 (due to charge conservation)


(II) LOOP RULE: zero net voltage drop around closed loop
 $\sum_{\text{closed loop}} \Delta V = 0$

RC Circuits: NEW CIRCUIT ELEMENT "Capacitor"

Any two (or more) conductors, which are held at a certain voltage difference produce an electric field, i.e. they carry a certain amount of charge. How much: CAPACITANCE


$$C = Q / \Delta V$$

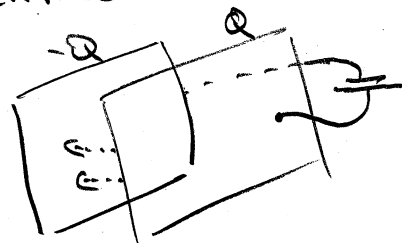For two large parallel plates
 $C = \frac{\epsilon_0 A}{d}$
 ϵ_0 - natural constant from Coulomb's law
 d - distance
 A - area of plates



$$[C] = \frac{C}{V} = F$$

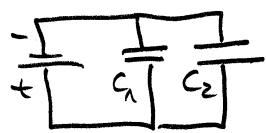When connected to battery you "fill up" capacitor with charge. Once "full" no more charge flows.




in parallel: total charge is sum of charges

$$Q_{\text{tot}} = Q_1 + Q_2$$

$$\Rightarrow C_{\text{tot}}^{\text{par}} = \frac{Q_1 + Q_2}{\Delta U} = C_1 + C_2$$
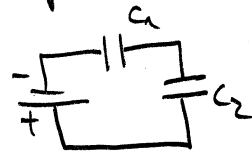
$$\Rightarrow \frac{1}{C_{\text{tot}}^{\text{series}}} = \frac{\Delta U}{Q} = \frac{\Delta U_1 + \Delta U_2}{Q} = \frac{1}{C_1} + \frac{1}{C_2}$$



in series: charge flow onto C_1 same as on C_2 . Total potential difference must be the sum (Kirchhoff)

$$\Delta U_{\text{tot}} = \Delta U_1 + \Delta U_2$$

"Capacitors store electric energy". To "fill up" capacitor from charge 0 to charge Q : $dW = dQ \cdot \Delta U = dQ \frac{Q}{C}$

$$W = \int dQ \frac{Q}{C} = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} Q_{\text{max}} \frac{\Delta U_{\text{max}}}{C} = \frac{1}{2} C (\Delta U_{\text{max}})^2$$

"Amount of charge that can be stored increases significantly if a non-conducting (dielectric) material is inserted between capacitor plates." Reason: electric dipoles in the material align and reduce the electric field generated by ΔU .

Now combine CAPACITOR and RESISTOR to explore charging & discharging:

Via Kirchhoff: $\mathcal{E} - \frac{Q(t)}{C} - I(t)R = 0$



• at $t=0$ no charge on capacitor, offers no potential to work against: $\mathcal{E}/R = I(0)$

• when capacitor full no more current and max charge

$$\mathcal{E} = Q_{\text{max}}/C \Rightarrow Q_{\text{max}} = C\mathcal{E}$$

Now analyze behavior over time: $I = \frac{dQ}{dt} \Rightarrow \frac{dQ}{dt} = \frac{\mathcal{E}}{R} - \frac{Q(t)}{RC}$


let's solve this: $\frac{dQ}{dt} = \frac{\mathcal{E}}{R} - \frac{Q}{RC}$ • move all reference to Q on LHS and all reference to t on RHS

$$\Leftrightarrow \frac{dQ}{\mathcal{E}C - Q} = \frac{dt}{RC} \cdot \text{integrate} \quad \int_{Q(0)}^{Q(t)} \frac{dQ}{\mathcal{E}C - Q} = \int_0^t \frac{dt}{RC} \quad \cdot \text{substitute } y = \mathcal{E}C - Q$$

$$-\left(\log(\mathcal{E}C - Q) - \log(\mathcal{E}C)\right) = \frac{1}{RC}(t-0) \Rightarrow \log\left(\frac{\mathcal{E}C - Q}{\mathcal{E}C}\right) = -\frac{t}{RC}$$

$$\frac{Q - \epsilon C}{-\epsilon C} = \exp[-t/RC] \Rightarrow \boxed{Q(t) = \epsilon C - \epsilon C e^{-t/RC} = \epsilon C (1 - e^{-t/RC})}$$

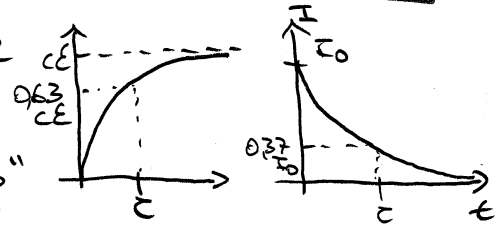accompanying current $I = \frac{dQ}{dt} = \frac{\epsilon C}{RC} e^{-t/RC}$




Time constant: $\tau = RC$ "how fast does it fill up"

$$[RC] = \Omega \cdot F = \cancel{V} \cdot \cancel{C} / \cancel{V} = C/A = C/Cs = s \checkmark$$

Discharging: remove battery from circuit and let charge flow between capacitor plates: $-Q/C - IR = 0 \Rightarrow Q(t) = Q_{max} e^{-t/RC}$

$$I(t) = -Q/RC \exp(-t/RC)$$

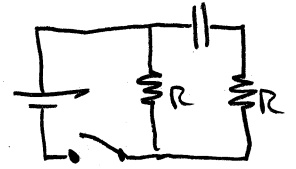

Quick check: ① just after switch closes what current flows in the battery? since no Q in capacitor $\Delta V_C = 0$
 via Kirchhoff $\Delta V_{R1} = \Delta V_{R2} = \epsilon \Rightarrow$ resistors in parallel
 $1/R_{tot} = 1/R_1 + 1/R_2 = 2/R \Rightarrow I = \epsilon/R_{tot} = 2\epsilon/R$

② when capacitor filled up: no current through outer loop
 $I = \epsilon/R$


FINAL ELEMENT: INDUCTOR (especially solenoid)

Closely connected to Faraday's law of INDUCTION: An electromotive force \mathcal{E}_{ind} is induced by time varying magnetic

Hint: $\mathcal{E} = - \frac{d\Phi_B}{dt}$ $\Phi_B = \vec{B} \cdot \vec{A}$ (either \vec{B} changes or \vec{A} changes)





$$\Phi_B = B \cdot A \cdot \cos\theta$$

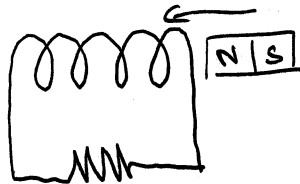


induces a current $I = \frac{\mathcal{E}_{ind}}{R}$
 what is direction of current?

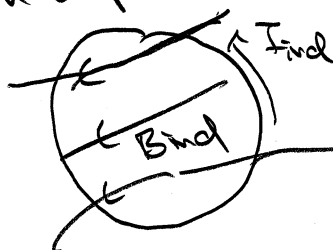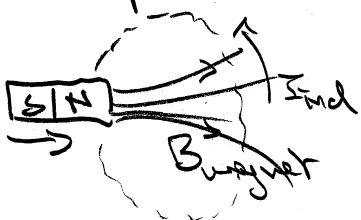Lenz's law: Induced current in the loop is in the direction that creates a magnetic field that opposes the change in magnetic flux through loop.



Necessary consequence: if a current is induced in a conductor there must be an electric field present that moves the charges.

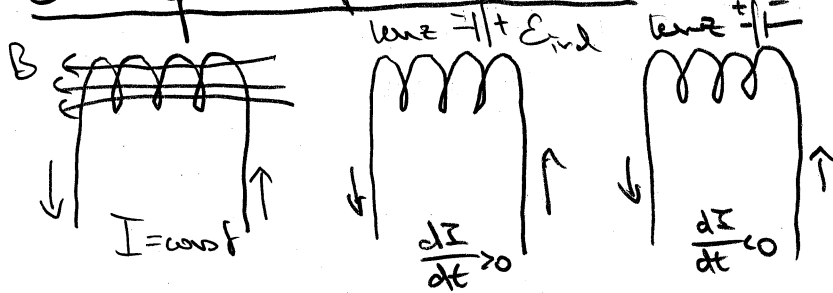Consequence for circuits: SELF INDUCTANCE



inductance

$$\mathcal{E}_L = -L \frac{dI}{dt}$$


with Faraday: $\mathcal{E}_L = -N \frac{d\Phi_B}{dt}$

of loop in solenoid

$$\Rightarrow L_{\text{solenoid}} = \frac{N\Phi_B}{I} \quad [L] = H \text{ "Henry"}$$

"Solenoid opposes changes in the current"

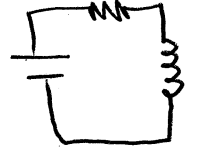Energy associated with mag. field in solenoid:




$$\mathcal{E} - IR - L \frac{dI}{dt} = 0 \quad \text{multiply by } I$$

$$I\mathcal{E} = IR^2 - LI \frac{dI}{dt}$$

power supplied by battery power dissipated by R power assoc with ind.


$$\frac{dE}{dt} = LI \frac{dI}{dt} \quad \boxed{E = \int dE = \int_0^I LI dI = \frac{1}{2} LI^2}$$

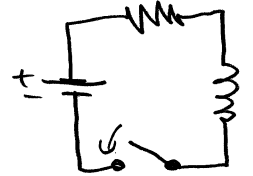RL circuit: when switched on similar analysis as for RC circuit for Q, here for I




$$I(t) = \frac{\mathcal{E}}{R} (1 - e^{-t \cdot R/L}) \quad \text{time constant } \tau = L/R$$

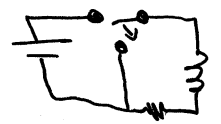
switching off: $I(t) = \frac{\mathcal{E}}{R} e^{-t/\tau}$



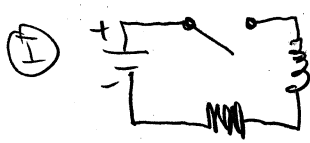Cross-checks: ① just after closing switch, across which circuit element is the voltage equal to the battery emf.
 ② after a long time? ① $t=0$ no current $\Delta V_R = 0$
 so with Kirchhoff $\Delta V_L = \mathcal{E}$ ② $t \rightarrow \infty$ $I = \text{const}$ in



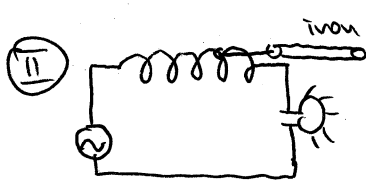solenoid so $\mathcal{E}_{\text{ind}} = 0 \Rightarrow \Delta V_R = \mathcal{E}$



Assume sinusoidal power source. When inserting metal bar B field inside solenoid increases, L increases. what happens to brightness of bulb?

Kirchhoff: $\mathcal{E} - L \frac{dI}{dt} - IR = 0 \rightarrow$ since L increases more voltage drop over solenoid, less drop over lamp \rightarrow dimmer

Oscillations in an LC circuit: electromagnetic analog
to a block on a spring on frictionless surface. (Electric energy
= potential energy and magnetic energy = kinetic energy)

Energy accounting $E_C = \frac{1}{2} Q^2 / C$ $E_I = \frac{1}{2} L I^2$

Energy conservation: $0 = \frac{d}{dt} E_{tot} = \frac{d}{dt} \left(\frac{Q^2}{2C} + \frac{1}{2} L I^2 \right) = \frac{Q}{C} \frac{dQ}{dt} + L I \frac{dI}{dt}$

since $I = \frac{dQ}{dt}$ and $\frac{dI}{dt} = \frac{d^2Q}{dt^2} \Rightarrow \boxed{\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q(t)}$

same form as $\frac{d^2x}{dt^2} = -\frac{k}{m} x = -\omega^2 x$ "oscillations in amount of
charge on capacitor plates with angular frequency $\omega = \sqrt{1/LC}$ "

Solution requires INITIAL CONDITIONS: e.g. fully charged
capacitor: $Q(0) = Q_{max}$ $I(0) = 0 \Rightarrow Q(t) = Q_{max} \cos(\omega t)$


$I(t) = -Q_{max} \omega \sin(\omega t)$ Sanity check:

$E_{tot} = \frac{1}{2C} Q_{max}^2 \cos^2(\omega t) + \frac{1}{2} L Q_{max}^2 \omega^2 \sin^2(\omega t) = \frac{Q_{max}^2}{2C} (\cos^2 + \sin^2) = \frac{Q_{max}^2}{2C}$

RLC circuit "Damped harmonic oscillations"

Energy conservation $\frac{d}{dt} (E_C + E_I + E_R) = 0$ $\frac{dE_R}{dt} = -I^2 R$

"dissipate power"

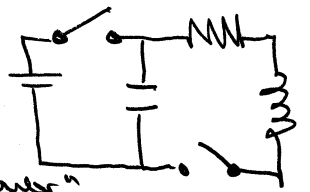

$L I \frac{d^2Q}{dt^2} + I^2 R + \frac{Q}{C} I = 0$

$\Rightarrow L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \Leftrightarrow m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = 0$ ANALOGOUS

for small R: $Q(t) = Q_{max} e^{-\frac{R}{2L}t} \cos(\omega_d t)$ $\omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$

AC Circuits Power source produces $V(t) = V_{max} \cdot \cos(\omega t + \phi)$

Use of complex numbers allows us to deploy similar techniques
as for DC circuits.



Promote to complex values $V(t) \mapsto \tilde{V}(t) = \tilde{V}_0 e^{i\omega t}$ $\tilde{V}_0 = V_{max} e^{i\phi}$

Physical voltage described by its REAL PART $V(t) = \text{Re}\{\tilde{V}(t)\}$

I Resistors in AC circuits

Its voltage drop follows that of the source instantaneously
i.e. voltage and current are IN PHASE
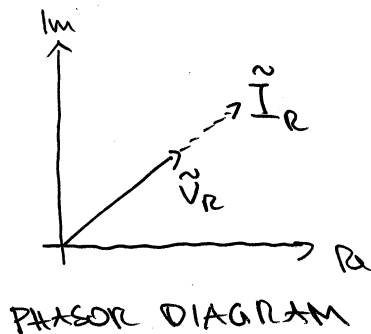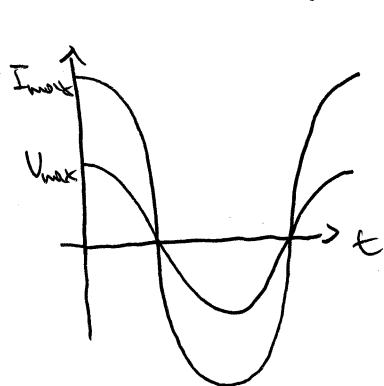
$$V_R(t) = U_{max} \cos(\Omega t + \phi) \quad R = V/I \Rightarrow I_R(t) = U_{max}/R \cos(\Omega t + \phi)$$



"complex Ohm's law"

$$\vec{V}_R = Z_R \cdot \vec{I}_R$$

here $Z_R = R$ purely real

"Z complex IMPEDANCE"

instead of I_{max} often quoted root-mean-square current:
average current over one cycle

$$I_{rms} = \sqrt{\overline{I^2}} \quad \text{with } \overline{I^2} = \int_0^T dt I_{max}^2 \sin^2(\Omega t) = \frac{1}{2} I_{max}^2 \quad \text{via } \sin^2(t) = \frac{1}{2} - \frac{1}{2} \cos(2t)$$

$$I_{rms} = I_{max} / \sqrt{2} = 0.707 I_{max}$$



II Inductors in AC circuits

Via Kirchhoff $V(t) - L \frac{dI}{dt} = 0$

i.e. if $V(t)$ is a cosine $I(t)$ is a sine.

"Solenoids oppose changes in current", so
that current lags voltage by $\phi = \pi/2$
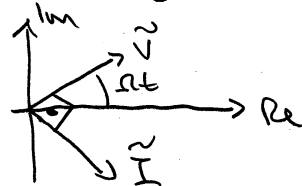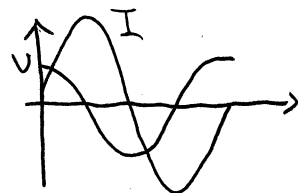
$$\text{implied via } \boxed{Z_L = i\Omega L}$$



III Capacitors in AC circuits



With Kirchhoff $V + Q/C = 0 \Rightarrow$

$$\Rightarrow I = \frac{dQ}{dt} = C U_{max} \Omega \sin(\Omega t + \phi)$$


"charges must flow onto capacitor for voltage to arise". Current ahead of
voltage by $\pi/2$

$$\boxed{Z_C = \frac{1}{i\Omega C}}$$
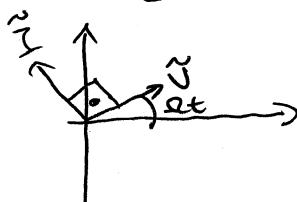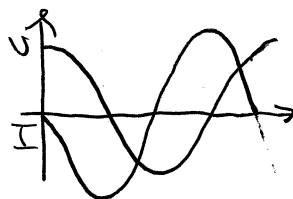
$$Q(t) = C U_{max} \cos(\Omega t + \phi)$$



RLC series circuit

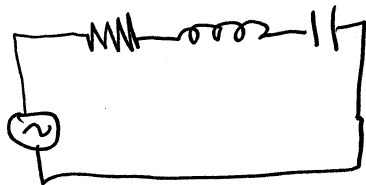

Since in series: CURRENT at all points must have the same amplitude and phase
⇒ Voltage across elements differs

With Kirchhoff: $\hat{V}(t) = V_{\max} e^{i\Omega t}$

$$L \frac{dI}{dt} + IR + \frac{Q}{C} = V_{\max} e^{i\Omega t}$$

ANALOG to driven and damped harmonic mechanical oscillator.

Steady state solution will oscillate with external Ω





Ansatz: $I(t) = I_0 e^{i\Omega t} \Rightarrow \dot{I}(t) = i\Omega I_0 e^{i\Omega t} \quad Q(t) = \frac{1}{i\Omega} I_0 e^{i\Omega t}$

$$(i\Omega L + R + \frac{1}{i\Omega C}) I_{\max} = V_{\max} \Rightarrow |I_{\max}| = \frac{|V_{\max}|}{|i\Omega L + R + \frac{1}{i\Omega C}|}$$

$$\Rightarrow |I_{\max}| = \frac{|V_{\max}|}{\sqrt{R^2 + (\Omega L - \frac{1}{\Omega C})^2}}$$

Maximum amplitude = RESONANCE
for $\Omega = 1/\sqrt{LC}$

In phasor diagram:

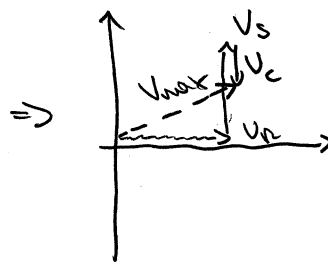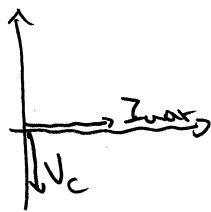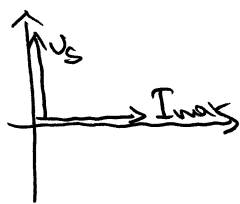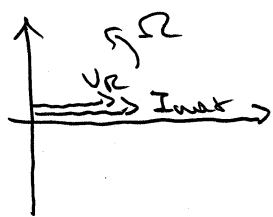

$$V_{\max} = \sqrt{V_R^2 + (V_C - V_C)^2} = I_{\max} \sqrt{R^2 + (\Omega L - \frac{1}{\Omega C})^2}$$

The smaller the resistance the sharper the resonance peak in I_{\max} as $\Omega \rightarrow 1/\sqrt{LC}$